


Raymond You

EECE 2160 Kimani

HW 5


1.

(i)

 

S	R	Q
0	0	no change
0	1	0
1	0	1
1	1	not allowed

(ii)

 


S	R	Q
0	0	no change
0	1	0
1	0	1
1	1	not allowed

(iii)
CLK

S

R

Q

 

S	R	Q
0	0	no change
0	1	0
1	0	1
1	1	not allowed


(iv)

CLK

S


R

Q

 


S	R	Q
0	0	no change
0	1	0
1	0	1
1	1	not allowed

 2. (10 points) Draw the timing diagram for the signal Q in the following circuit. Assume $Q=0$ initially, the S-R Flip Flop is unclocked, and it behaves as shown in problem 1 above.




w	x	S	R
0	0	0	0
0	1	0	0
1	0	0	1
1	1	1	0

 


S	R	Q
0	0	no change
0	1	0
1	0	1
1	1	not allowed

 3. (5 points) Complete the timing diagram for a trailing (falling) edge triggered J-K Flip-Flop.
Assume $Q=0$ initially.



Truth Table			
J	K	CLK	Q
0	0	↑	Q_0 (no change)
1	0	↑	1
0	1	↑	0
1	1	↑	\bar{Q}_0 (toggles)

4.

 

format: 0/1
0 is input
1 is output

truth table


x (current state)	y (input)	z (next state)	out
a	0	a	0
a	1	b	1
b	0	b	1
b	1	a	0

K-Map

	y	
	0	1
x	0	1
	0	1
	1	0

$$Out = xy' + x'y$$

$$Out = x \oplus y$$

 

← D flip-flop


5.

$$D_A = X'A + XY$$

$$D_B = X'A + XY$$

$$Z = XB$$

5. a) This is a sequential mealy circuit

 


b) State table

[illegible]


c) State diagram

00/0
↑
input output

 

A = 00
B = 01
C = 10
D = 11

6.

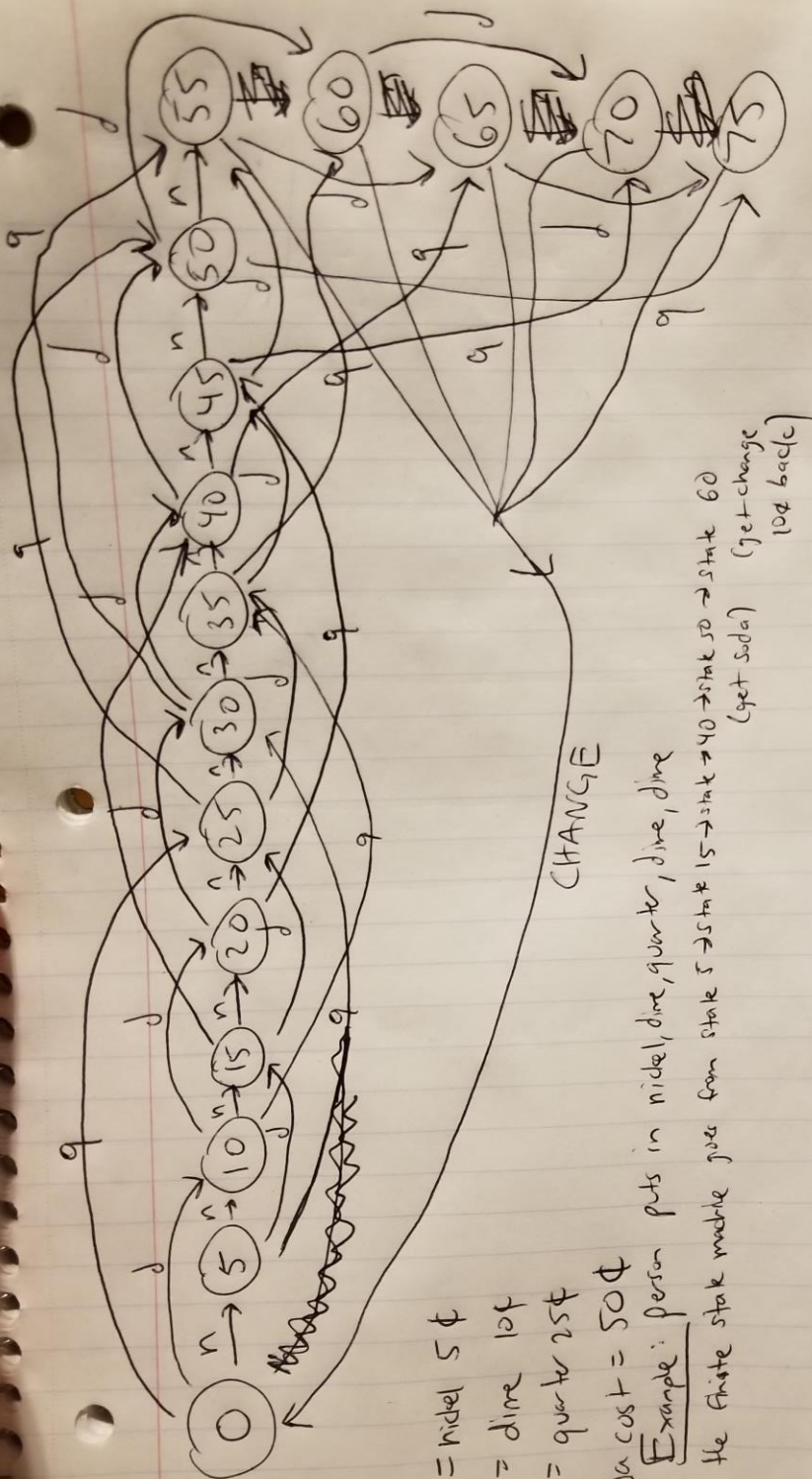

n = nickel 5¢
 d = dime 10¢
 q = quarter 25¢
 Soda cost = 50¢



Example: person puts in nickel, dime, quarter, dime, dime
 the finite state machine goes from state 5 → state 15 → state 40 → state 50 → state 60
 (get soda) (get change 10¢ back)

Another example: person puts in quarter, quarter, quarter

the FSM goes from state 25 → state 50 → state 75
 (get soda) (get change 25¢ back)

This is a MEALY Machine

7.

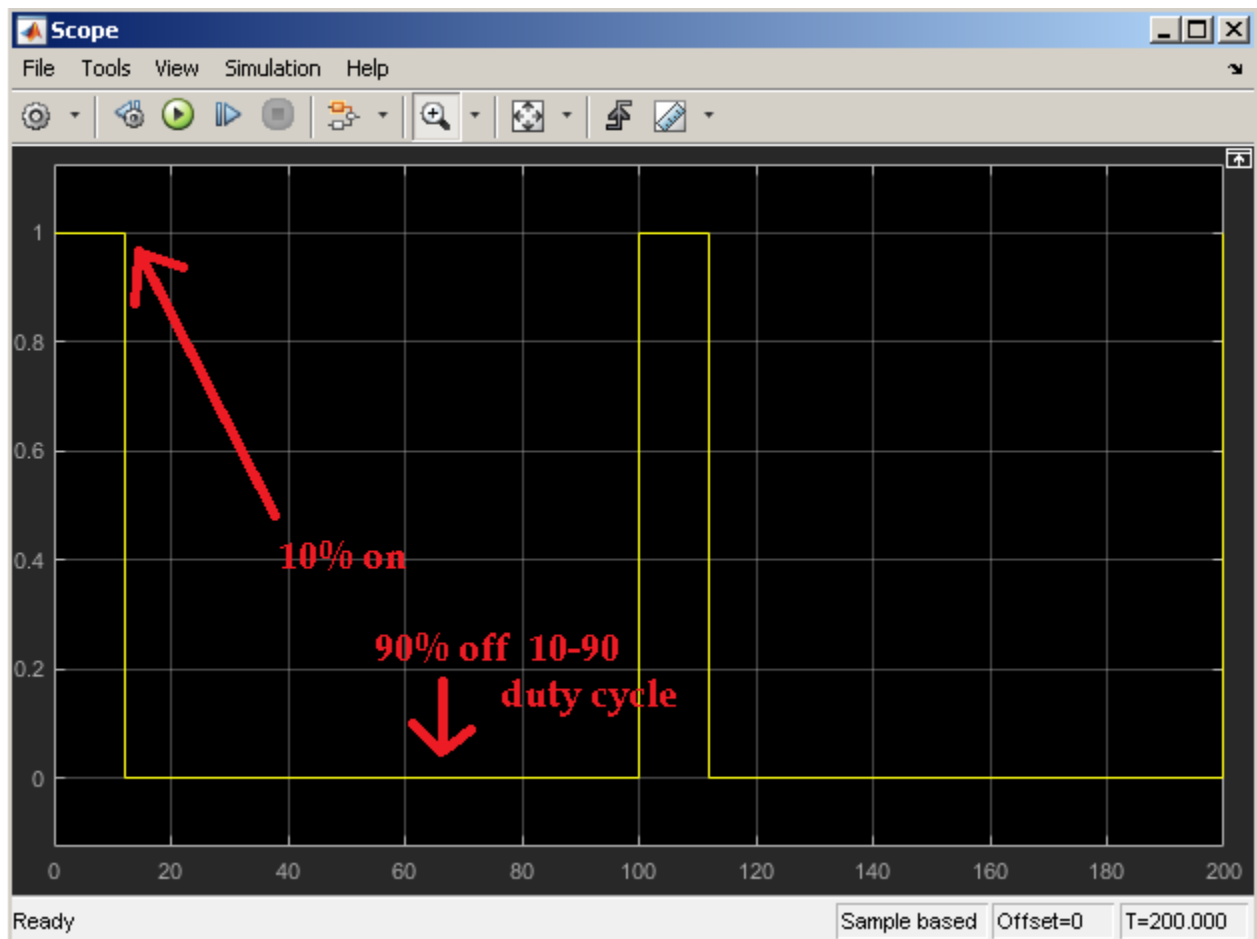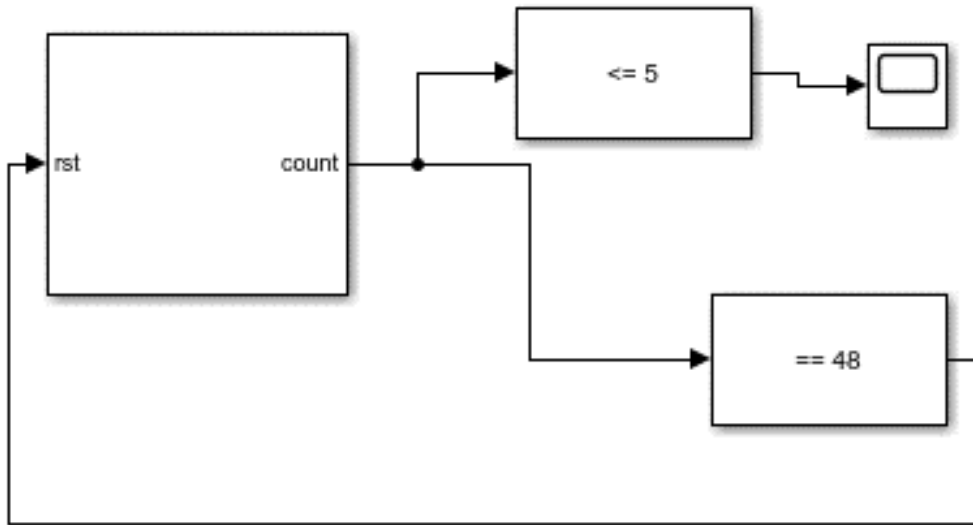

In the scope, it is generated for 2 cycles. Each cycle having 100 periods. Everything got scaled down to smaller number for simpler scoping purposes. The original values for the 2 gigahertz clock were: 1 ms was 2,000,000,000 cycles. This was based off of the zedboard which is 50 MHz and each ms in the zedboard is 50,000,000 cycles. The initial value of the counter is 0 and it goes up by step values of 2. Because the step values are 2, both the compare to constants are also halved. So the original compare to constants were 10 and 96. Now they are 5 and 48.